

See discussions, stats, and author profiles for this publication at: <https://www.researchgate.net/publication/317488825>

# Thevenin's Theorem and its Applications

Presentation · June 2017

DOI: 10.13140/RG.2.2.27671.57768

CITATIONS

0

READS

22,683

1 author:



Professor G R Sinha

Myanmar Institute of Information Technology Mandalay Myanmar

204 PUBLICATIONS 430 CITATIONS

SEE PROFILE

Some of the authors of this publication are also working on these related projects:



Breast Cancer [View project](#)



Reliable CAD system for Breast cancer detection [View project](#)

# Thevenin's Theorem and its Application

By

**Dr G R Sinha**

*IEEE Senior Member & Fellow IETE*

Professor, Department of Electronics and Communication Engineering


**CMR Technical Campus, Hyderabad**

# Outline of Lecture


- **Lecture Objectives**
- **Thevenin's Theorem**
- **Examples**
- **Application**
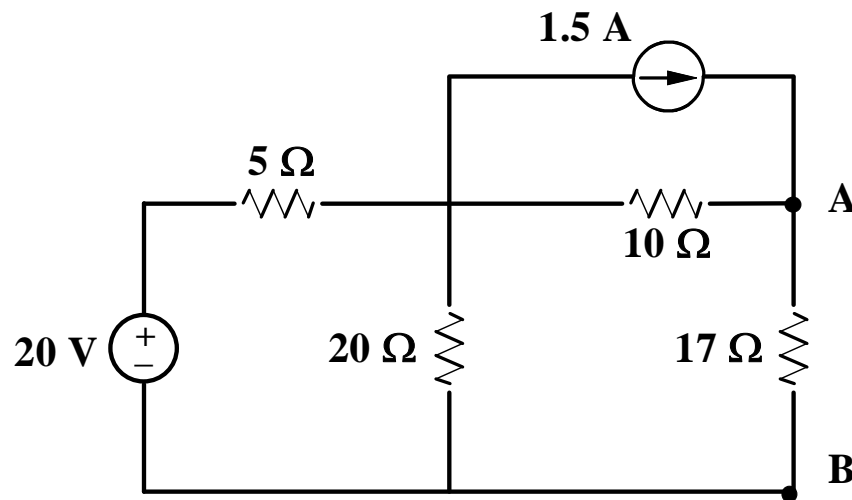
# Lecture Objectives

- To **understand Thevenin's theorem** and simplify electrical networks into simple equivalent circuits using the theorem.
- To study an **application of the theorem**.



1 An example of Network

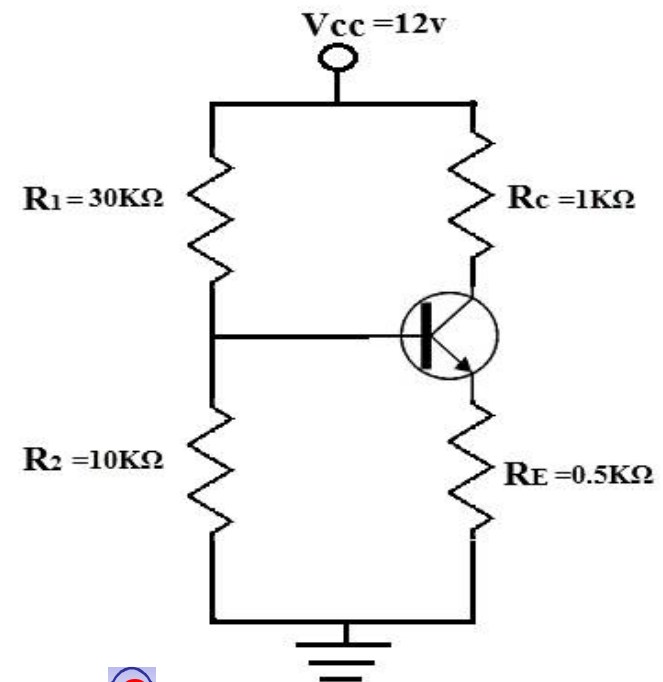


2 Transistor Circuit

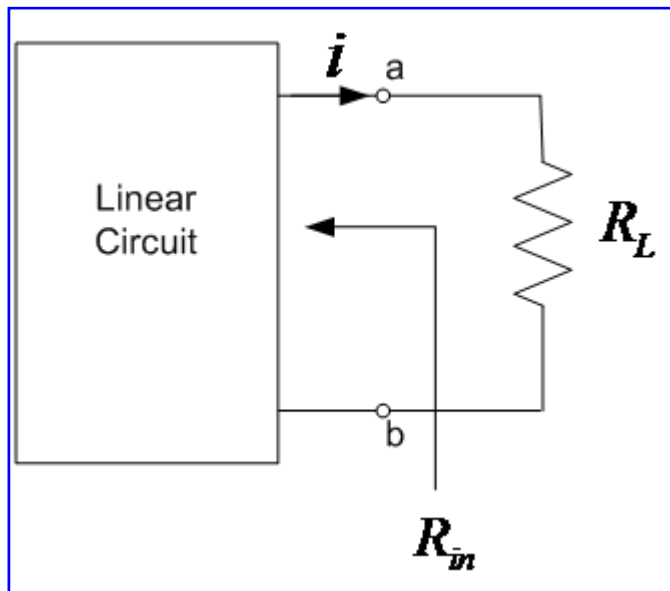
# Thevenin's Theorem

**Thevenin's theorem** states that a **linear and bilateral network** can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistance  $R_{Th}$ .

where  $V_{Th}$  is the open-circuit voltage across load terminals, and  $R_{Th}$  is the input or equivalent resistance at the terminals when all the independent sources are turned off.



1


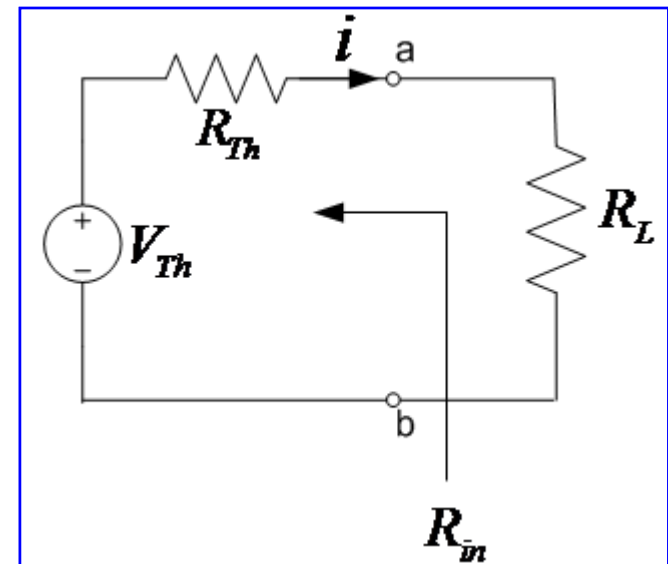


2

## Thevenin's Theorem (*contd..*)
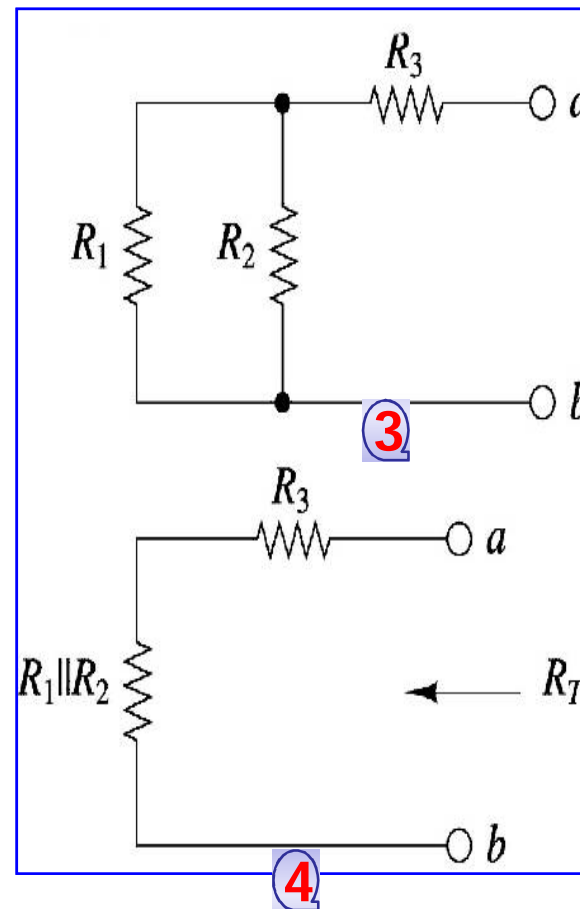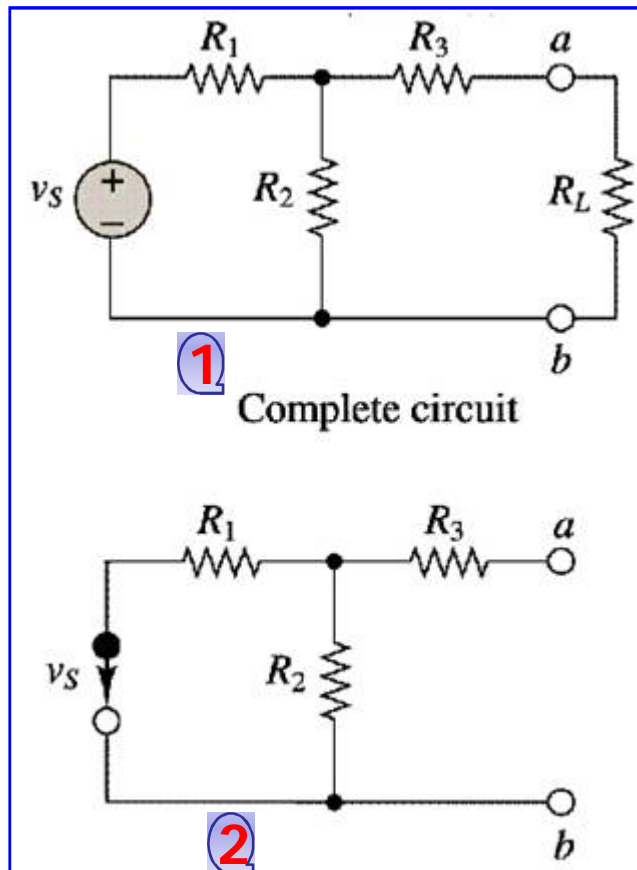
### Determination of $R_{Th}$ (Thevenin's Resistance):



The resistance seen by the load, with removed load and all **independent** sources turned off (Voltage sources replaced by short circuits & current sources replaced by open circuits).






## Thevenin's Theorem (*contd..*)
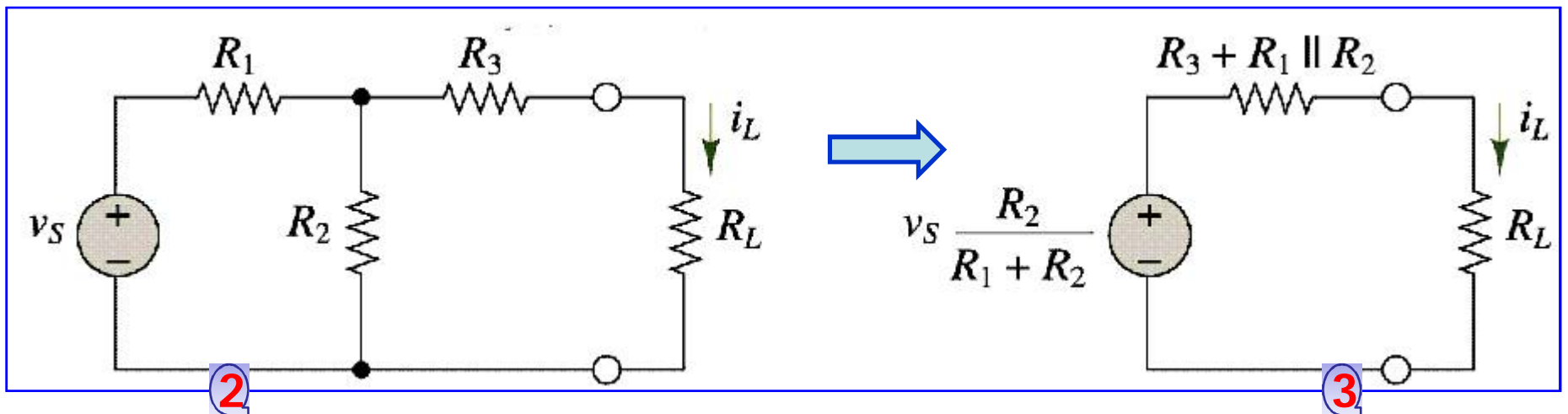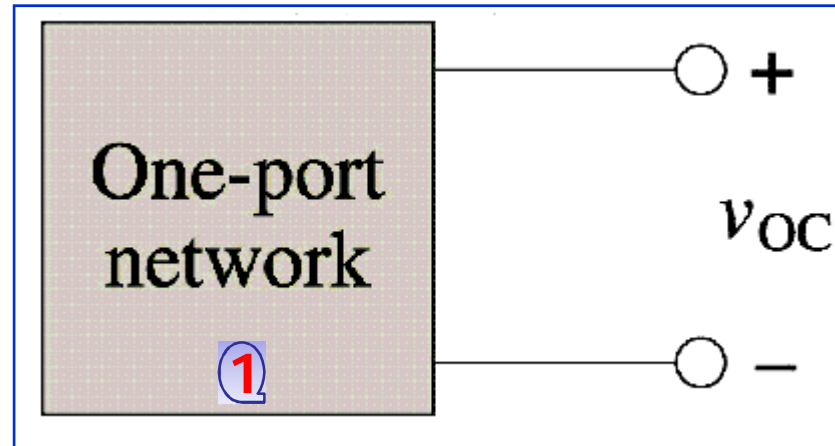
### **Determination of $V_{Th}$ (Thevenin's Voltage):**

The voltage across the load under open circuit condition, also called as open circuit voltage.





# Example # 1

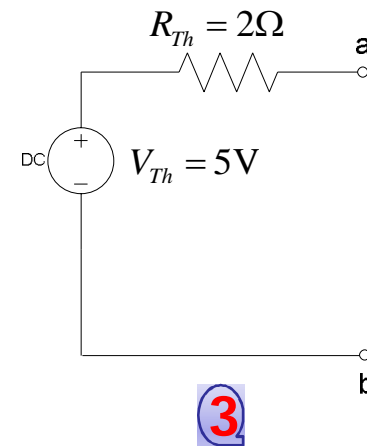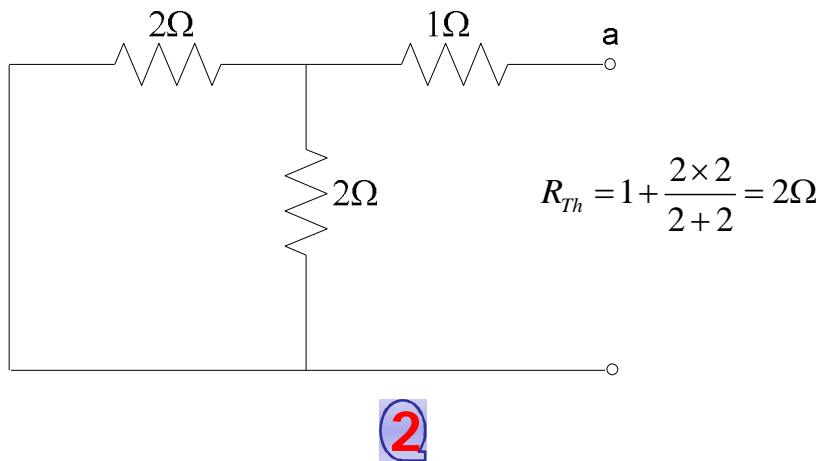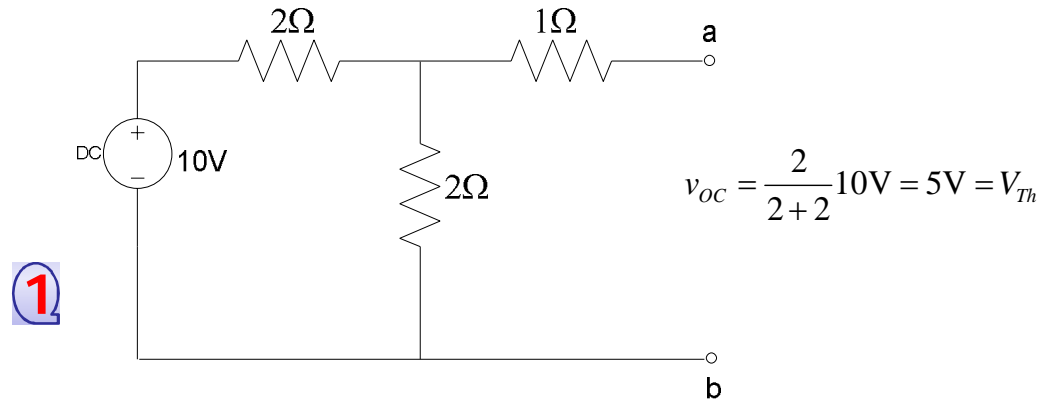




## Example # 2

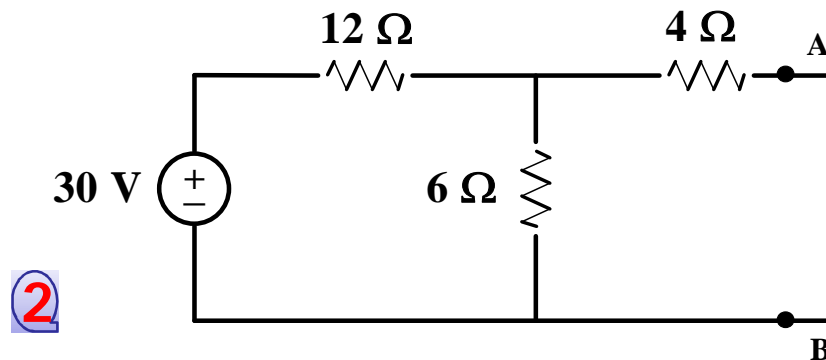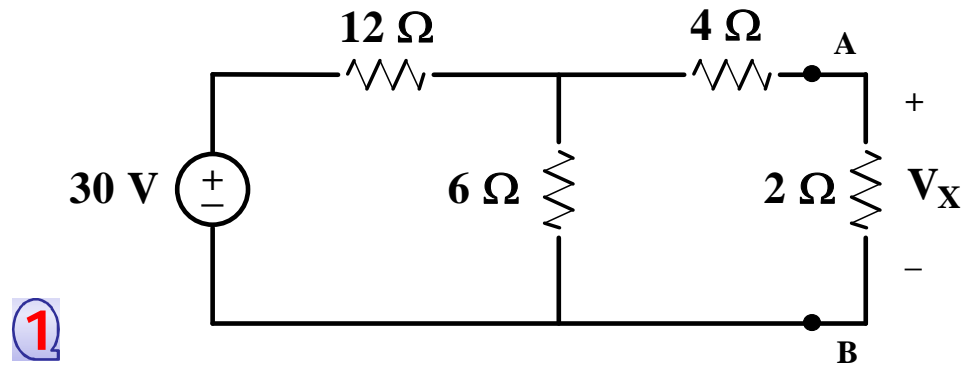


$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$

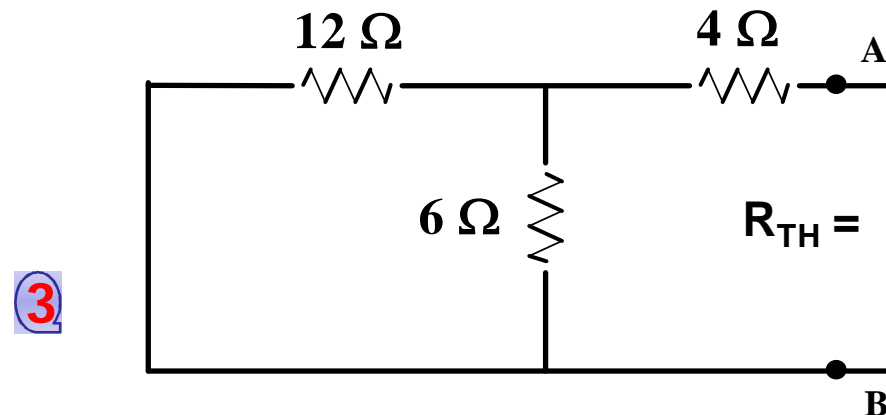



$$R_{TH} = 12 || 6 + 4 = 8 \Omega$$

## Example # 3

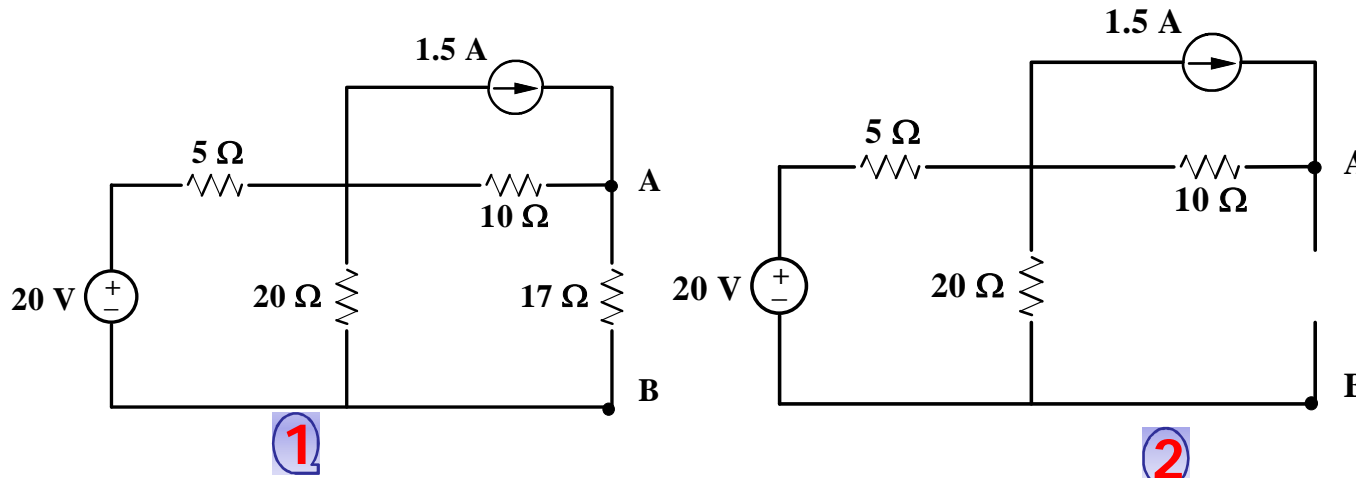


$$V_{AB} = V_{TH} = (1.5)(10) + \frac{20(20)}{(20+5)}$$

$$\therefore V_{TH} = 31V$$

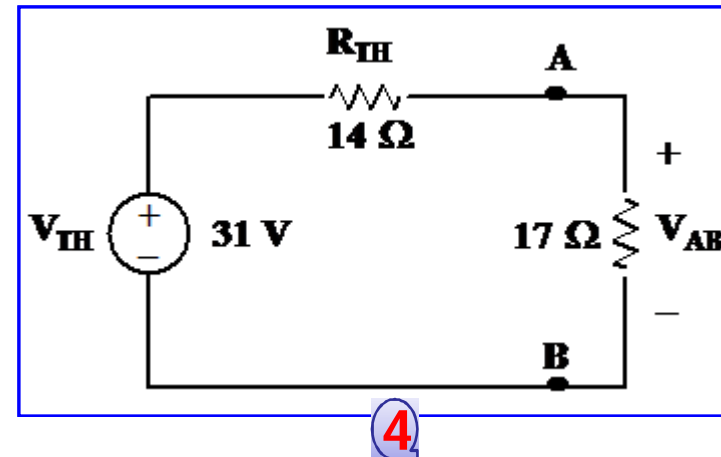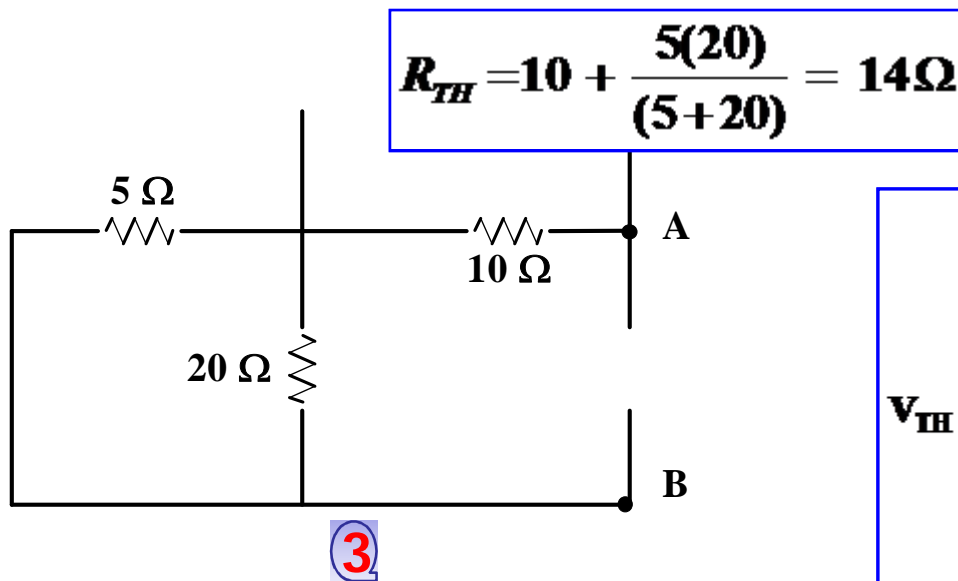

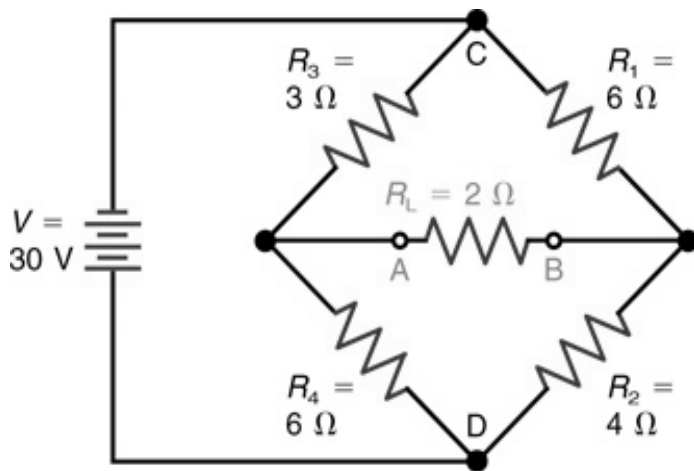
## Example # 4

Determining the voltage drop across  $R_L$




1

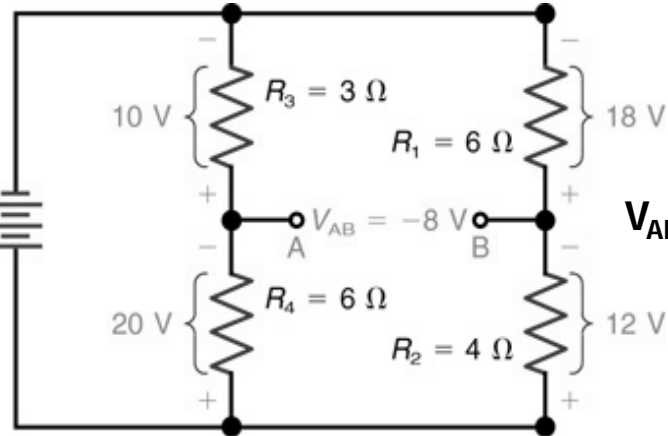


2

$$V_{AB} = -20 - (-12) = -8V$$
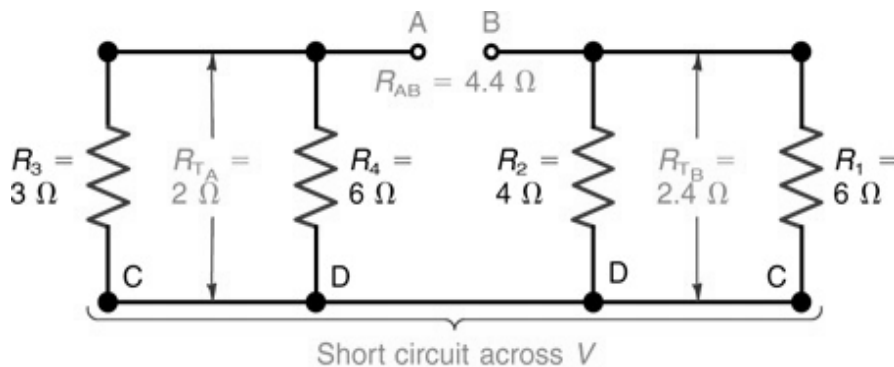
$$R_{Th} = R_{TA} + R_{TB} = 2 + 2.4 = 4.4 \Omega$$







3

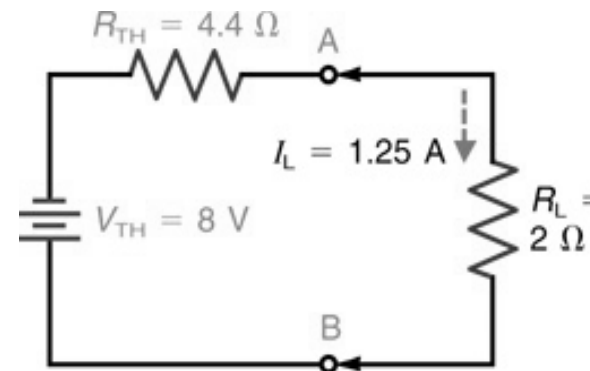

4
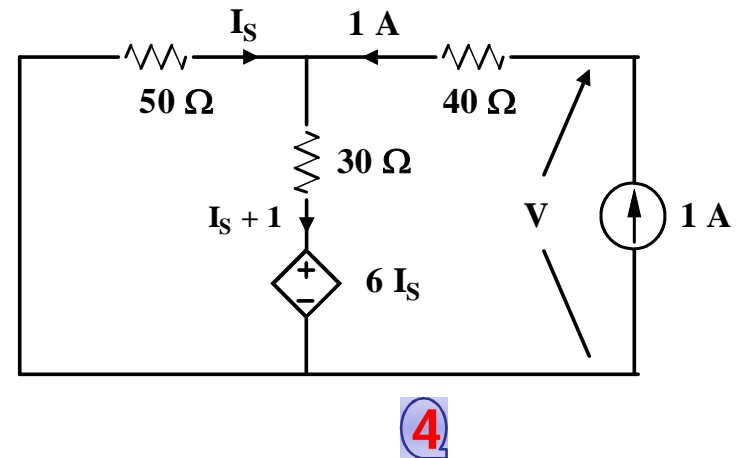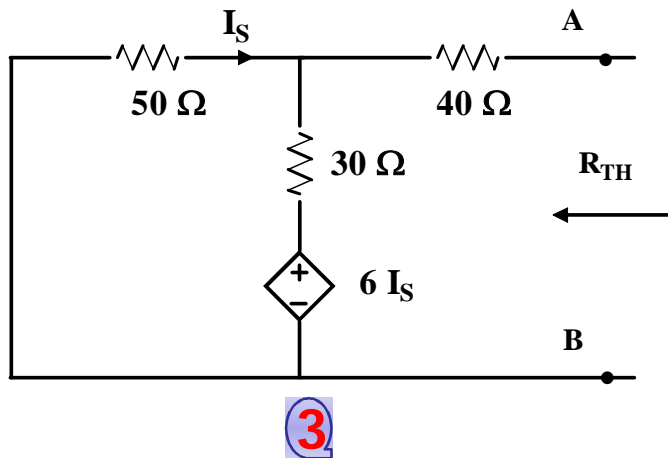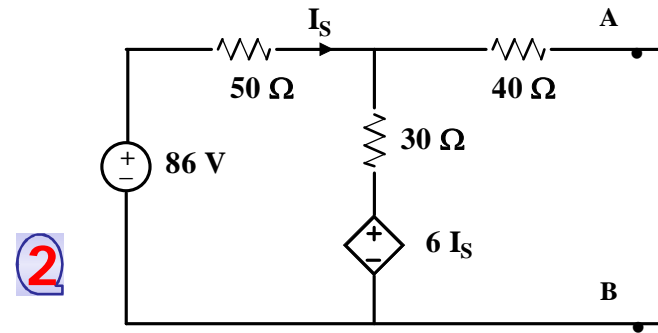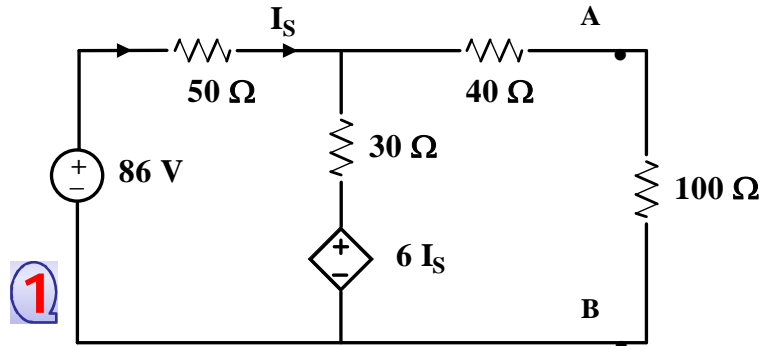
## Example # 5

Find the voltage across the  $100\ \Omega$  load.



$$50I_S + 30(I_S + 1) + 6I_S = 0$$


**2**

$$-86 + 80I_S + 6I_S = 0 \rightarrow I_S = 1\text{ A}$$

$$V_{AB} = 6I_S + 30I_S = \rightarrow 36\text{ V}$$

$$I_S = \frac{-15}{43}\text{ A}$$


## Example # 5 (contd..)

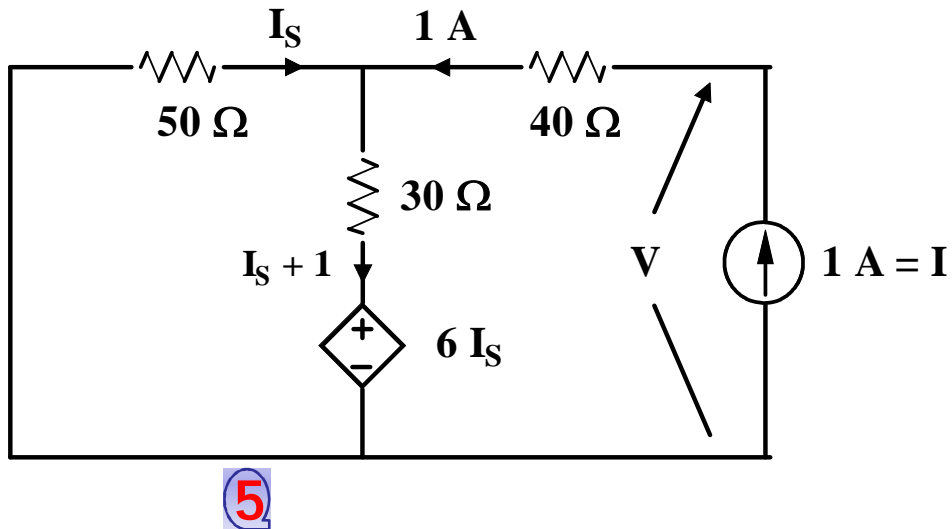

$$50 \left( \frac{-15}{43} \right) - 1(40) + V = 0$$

$$V = 57.4 \text{ volts}$$
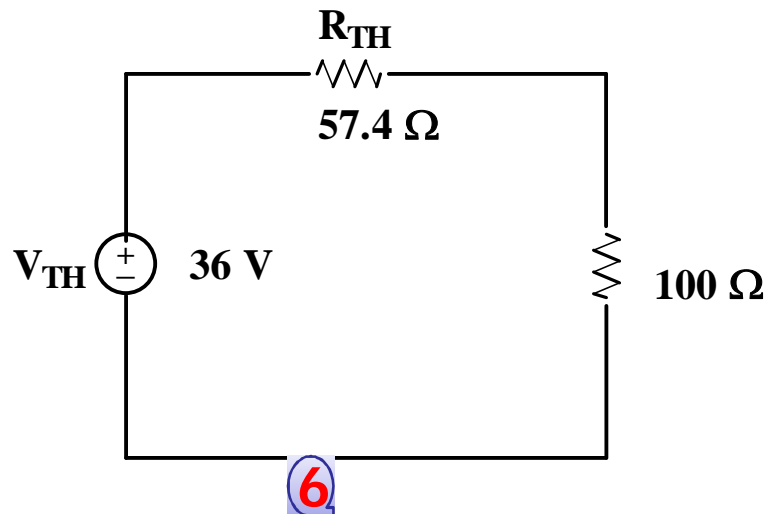
$$R_{TH} = \frac{V}{I} = \frac{V}{1} = 57.4 \Omega$$




$$V_{100} = \frac{36 \times 100}{57.4 + 100} = 22.9 \text{ V}$$

# Applications of Thevenin's Theorem

- To determine **Change in Load Voltage**: To predict range of load voltage variation due to change in load resistance.
- To obtain **Norton's equivalent circuit**.
- To determine **Maximum power** that can be transferred to Load from the network.
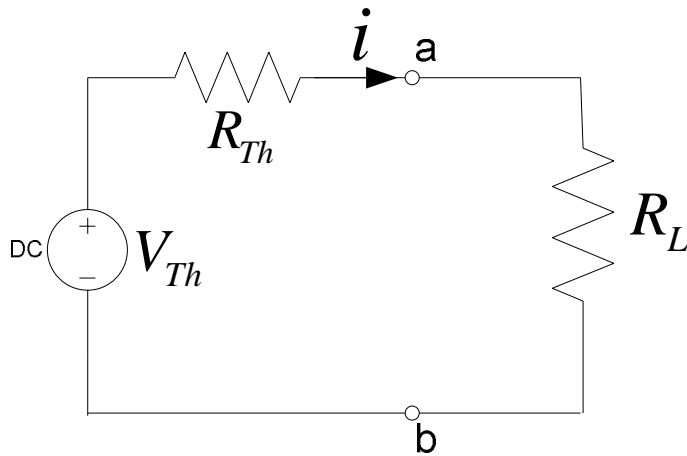
# Maximum Power Transfer Theorem

Maximum power transfer from a circuit to a variable load occurs when the load resistance equals the source resistance,  $R_L = R_{Th}$ .



$$p = i^2 R_L = \left[ V_{Th} / (R_{Th} + R_L) \right]^2 R_L$$

This power is maximum when

$$\partial p / \partial R_L = 0$$

This gives:  $R_L = R_{Th}$

$$p_{\max} = \left[ V_{Th} / (R_{Th} + R_L) \right]^2 R_L \Big|_{R_L = R_{Th}}$$

$$p_{\max} = \left[ V_{Th} / (2R_{Th}) \right]^2 R_{Th} = V_{Th}^2 / 4 R_{Th}$$

# Sincere Thanks with Inspiring Equation

$$E = mc^2$$

E = Excellence, m = Motivation, C = Commitment

$c = 0.5$ (Half hearted) $E = \frac{1}{4}$ $c = 2$ (Doubly enthused) $E = 4$
---