



Government Polytechnic Jalgaon

Academic Year 2019-20

Course Code

Digital Techniques(22230)

EJ 3 I.

TITLE

To study Design And Implementation Of Half Adder And Half Subtractor.

Submitted By :-

1. Prathamesh Saraf (13)
2. Rohit Koli (14)
3. Tushar Rathod (15)
4. Hiten Mahajan (16)

Under the guidance of:

MR C.R.bharhate(sir)

Rational :-

In the present scenario most of the electronics equipment like computers , mobiles , music systems , ATM , automation and control circuit and systems are based on digital circuit which the diploma electronics engineering passout (also called technologists) have to test them .

The knowledge of basic logic gate , combinational and sequential logic circuits using discrete gates as well as digital ICs will enable the student to interpret the working of equipment and maintain them. After completion of the course , students will be able to develop digital circuits based application .



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION Certificate

This is to certify that Mr/Ms.**Prathamesh, Rohit , Tushar , Hiten ,** Roll No.**13,14,15,16** Of **3rd** Semester of Diploma in **E&TC.** of Institute, **Government Polytechnic, Jalgaon** (Code:0018/1567) has completed the **Micro Project** satisfactorily in the Subject – **digital electronic (22320)** for the Academic Year 2019- 2020 as prescribed in the curriculum.

Place: **Jalgaon**

Enrollment No:-

1800180265,1800180.....,1800180..... , 1800180.... , 1800180.....


Date:-

Exam. Seat No:-

Subject Teacher

Head of the Department

Principal

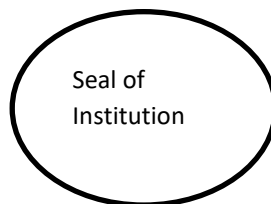

Seal of
Institution

Subtractor :-

The subtractor of two binary numbers can be done by taking the complement of the subtrahend and adding it to minuend .

The rules of subtractor of binary subtraction are as follows:

$$0 - 0 = 0$$

$$0 - 1 = 1 \text{ (borrow=1)}$$

$$1 - 0 = 1$$

$$1 - 1 = 0$$


There are two types of binary subtractors :

- 1 Half subtractor
- 2 Full subtractor

1 Half subtractor :-

The half subtractor is a combinational circuit with two inputs and two outputs.

Block diagram:-

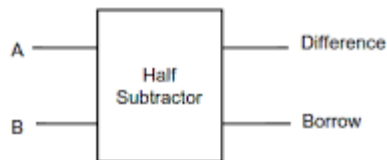

Truth table :-

Half Subtractor-Truth Table			
Input		Output	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K map:-

1 For difference :-

A \ B	0	1
0	0	1
1	1	0


$$\begin{aligned}\text{Difference} &= A\bar{B} + \bar{A}B \\ &= A \oplus B\end{aligned}$$

2 For borrow :-

A \ B	0	1
0	0	1
1	0	0

$$\text{Borrow} = \bar{A}B$$

Logic diagram :-

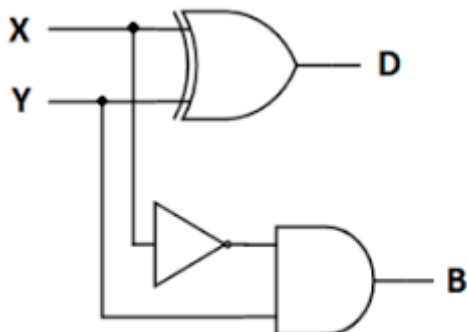

Application of Half Subtractor:-


The applications of half subtractor include the following.

- Half subtractor is used to reduce the force of audio or radio signals
- It can be used in amplifiers to reduce the sound distortion
- Half subtractor is used in ALU of processor
- It can be used to increase and decrease operators and also calculates the addresses
- Half subtractor is used to subtract the least significant column numbers. For subtraction of multi-digit numbers, it can be used for the LSB.

2. Full subtractor

The full subtractor is a combination circuit which performs subtraction between two bits considering that a 1 has been borrowed from the previous stage.

Block diagram:-

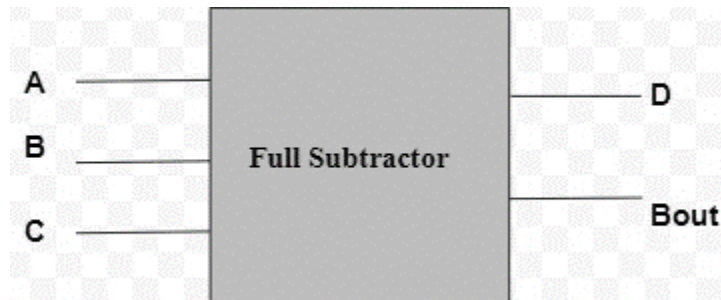

Truth table :-

Input			Output	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Kmap:-

For difference :-

A \ B _{in}	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$D = \overline{A}B\overline{B}_{in} + \overline{A}B\overline{B}_{in} + A\overline{B}\overline{B}_{in} + AB\overline{B}_{in}$$

For borrow:-

A \ B B _{in}				
	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$

Logic diagram

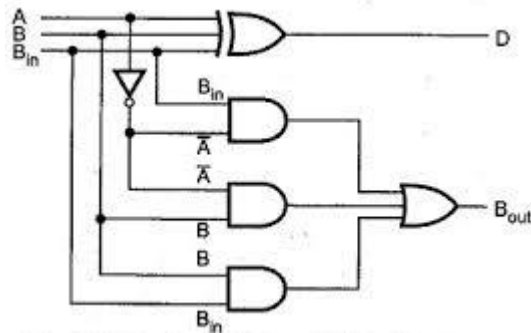

Application of full subtractor :-

- These are generally employed for ALU (Arithmetic logic unit) in computers to subtract as CPU & GPU for the applications of graphics to decrease the circuit difficulty.
- Subtractors are mostly used for performing arithmetical functions like subtraction, in electronic calculators as well as digital devices.
- These are also applicable for different microcontrollers for arithmetic subtraction, timers, and program counter (PC)
- Subtractors are used in processors to compute tables, address, etc.
- It is also useful for DSP and networking based systems.

